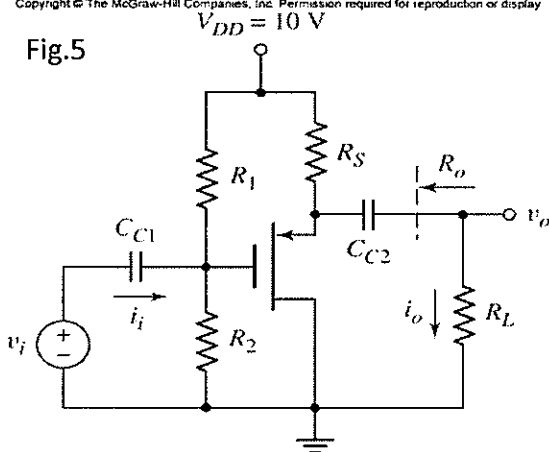


國立高雄海洋科技大學 105 學年度碩博士班考試入學
微電子工程系碩士班—微電子學試題
【※須使用計算機】

1. Why the direction of current density is consistent with the gradient of N type doping distribution (∇N or $\frac{\partial n}{\partial x \partial y \partial z}$) and is opposite with the gradient of P type doping distribution (∇P or $\frac{\partial p}{\partial x \partial y \partial z}$) 20%
2. As we know, a. All the drifting carriers (electrons and holes) can contribute drift current. b. In any type of semiconductor, both electrons and holes exist. Now, N type Si with $1 \times 10^{15}/\text{cm}^3$, why the drift current calculate only focuses on electrons? 10%
3. (a) plots the center-tapped rectifier and bridge rectifier circuits 10% (b) Under the same 220 V 60Hz ac source with $N_0 = 500$ turns peak voltage output voltage $V_O = 12$ V and the same diode cut-in voltage $V_r = 0.7$ V, compare the turns requested, PIV of diode at each rectifier. 20%
4. For the transistor in the circuit in Fig. 4, the parameters are $V_{TN} = 0.4$ V and $k'_n = 0.12 \text{ mA/V}^2$ and $W/L = 25$. Determine V_{GS} , I_D and V_{DS} 20%. Sketch the load line and plot the Q-point. 20%
5. In Fig. 5, $R_S = 4\text{k}\Omega$, $R_1 = 850\text{k}\Omega$, $R_2 = 350\text{k}\Omega$ and $R_L = 4\text{k}\Omega$. The transistor parameters are $V_{TP} = -1.2$ V and $k'_p = 0.04 \text{ mA/V}^2$, $W/L = 80$, and $\lambda = 0.05\text{V}^{-1}$. Find (a) I_{DQ} and V_{SDQ} (b) A_v (c) R_O . 30%


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

Fig.5



Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

Fig.4

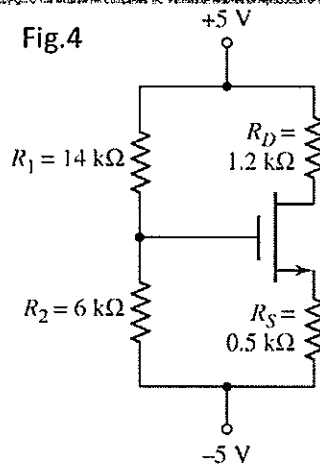

< 試題結束 >